

EEE103 / EEE121 / EEE141 Problem Sheet Solutions

Diode Conduction State:

Q1 Solutions are only provided for those problems that are given with a numerical answer.

(a) -


(b) - make an assumption; here it will be assumed that the diode is not conducting so diode must be replaced by an open circuit....

must find V_A and V_C w.r.t. reference....

$V_A = 6V$

$V_C = 4V$ (no volts are dropped across R)

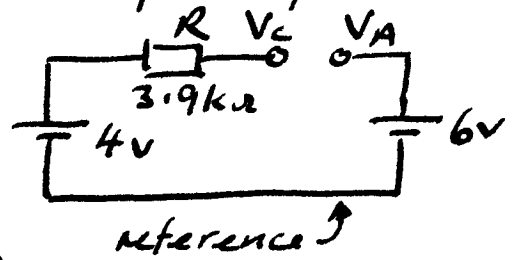$\therefore V_A - V_C = 2V \Rightarrow$ diode conducts; assumption wrong.




- now must recalculate to find forward bias current....

since this is a series loop, simplest way to proceed is add up voltage around loop....

$4V + I_D R + 0.7V - 6V = 0$

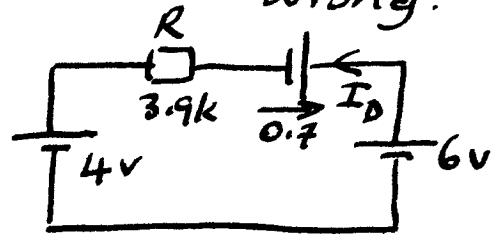
or $I_D = \frac{6 - 4 - 0.7}{3.9k} = \underline{\underline{0.33mA}}$



(c) -

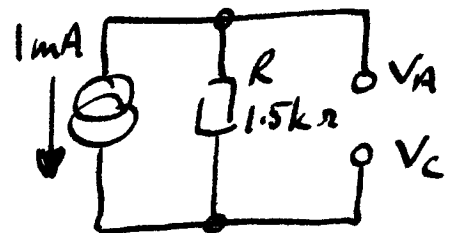(d) - assume diode not conducting as in (b)

$V_A - V_C =$ volts across R
 $= -1mA \times 1.5k$
 $= \underline{\underline{-1.5V}}$




\therefore diode reverse biased by $1.5V \Rightarrow$ assumption is correct.

(e) - assume diode not conducting ...

$$V_A = 2\text{mA} \times 12\text{k}\Omega = 24\text{V}$$

$$V_C = 9\text{mA} \times 2.2\text{k}\Omega = 19.8\text{V}$$
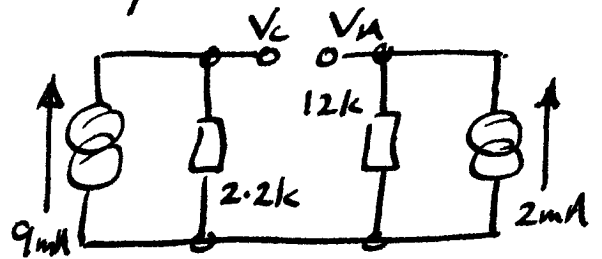
$$V_A - V_C = 24 - 19.8 = \underline{\underline{4.2\text{V}}}$$



∴ assumption wrong; diode conducts.


- now replace diode by a 0.7V source ...

using superposition..

$$I_D(0.7\text{V}) = -0.7 / 14.2\text{k}\Omega$$

$$I_D(9\text{mA}) = - \frac{9\text{mA} \cdot 2.2\text{k}}{14.2\text{k}}$$
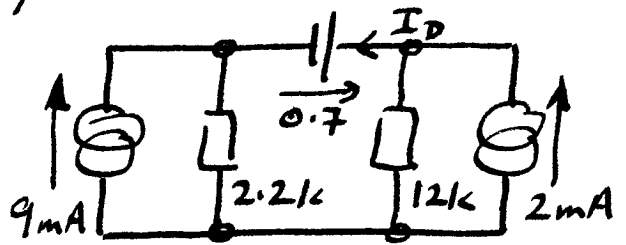
$$I_D(2\text{mA}) = + \frac{2\text{mA} \cdot 12\text{k}}{14.2\text{k}}$$



$$I_{TOT} = \frac{1}{14.2\text{k}} [-0.7 - 19.8 + 24] = \frac{3.5\text{V}}{14.2\text{k}\Omega} = \underline{\underline{246\mu\text{A}}}$$

Note that converting the combinations (9mA, 2.2k) and (2mA, 12k) into Thevenin equivalents yields a single loop that can be solved easily as in (b).

(f) -

(g) -

Q2 In all the examples of Q2, the condition $V_D = 0.7\text{V}$, $I_D = 0$ is required so assume a conducting diode, find I_D in terms of variable source then put $I_D = 0$.


Alternatively replace diode by an open circuit and find out the value of source that will give $V_A - V_C = 0.7\text{V}$.

(a) - The loop equation for this circuit is ...

$$0.7V + V + I_D 1k\Omega = 0$$

if $I_D = 0$,
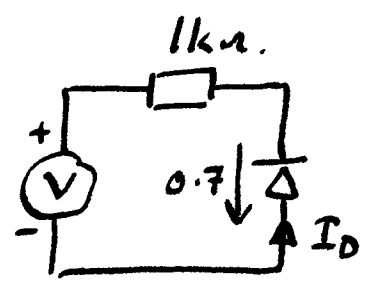
$$0.7 + V = 0 \text{ or } \underline{\underline{V = -0.7V}}$$




(b) - The loop equation for this circuit is ...

$$V + I_D 3.9k\Omega + 0.7 - 6 = 0$$

and if $I_D = 0$,
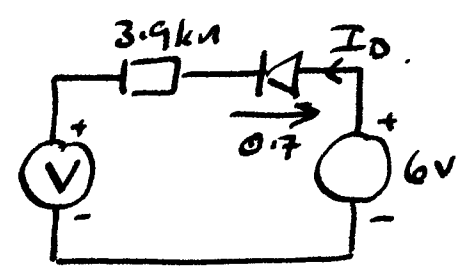
$$V = 6 - 0.7 = \underline{\underline{5.3V}}$$



(c) - voltage across 1k resistor is 0.7V so ...

$$I_R = 0.7 / 1k\Omega = 0.7mA$$


summing currents at diode's anode node ...

$$I_T = I_R + I_D = \frac{V - 0.7}{3.3k\Omega}$$

and putting $I_D = 0$...

$$I_R = 0.7 / 1k\Omega = \frac{V - 0.7}{3.3k\Omega}$$
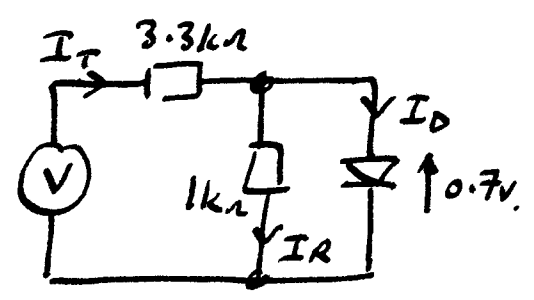
$$\text{or } V = \frac{0.7 \times 3.3}{1} + 0.7 = \underline{\underline{3.01V}}$$



(d) - voltage across 1.5k resistor is 0.7V so ...


$$I_R = 0.7 / 1.5k\Omega$$

summing currents at diode anode node ...

$$I + I_R + I_D = 0 = I + 0.7 / 1.5k\Omega + I_D$$

if $I_D = 0$,
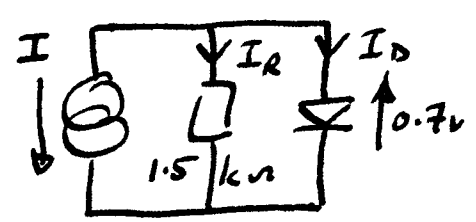
$$I + 0.7 / 1.5k\Omega = 0 \text{ or } I = -\frac{0.7}{1.5k\Omega} = \underline{\underline{-0.467mA}}$$



(e) - using loops ...

$$0.7V + (I_D - I_2) 2.2k\Omega + (I_D - I) 12k\Omega = 0.$$


but $I_2 = -9mA$

$$\therefore 0.7V + 2.2k\Omega I_D + 12k\Omega I_D + 19.8V - I \cdot 12k\Omega = 0$$

and if $I_D = 0$

$$0.7V + 19.8V - 12k\Omega I = 0$$
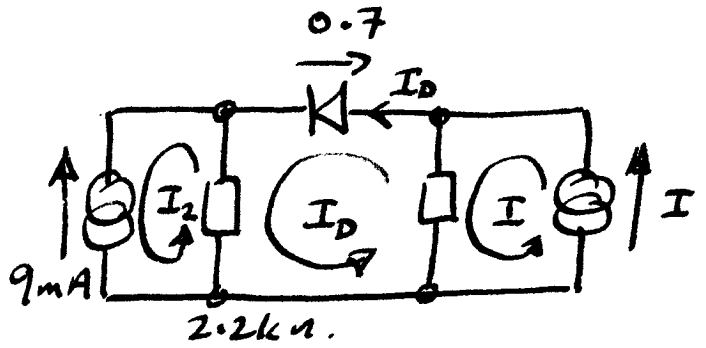
$$\text{or } I = \frac{0.7V + 19.8V}{12k\Omega} = + \frac{20.5}{12k\Omega} = + \underline{\underline{1.71mA}}$$




(f) - using loops

$$-V + 0.7 + (I_D + 0.6) \cdot 12 = 0$$

if $I_D = 0$...


$$-V + 0.7 + 7.2 = 0.$$
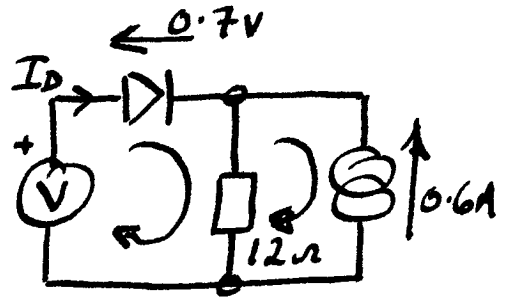
$$\text{or } \underline{\underline{V = 7.9V}}$$



(g) - since volts across 3kΩ is 0.7V,

$$I_R = 0.7 / 3k\Omega.$$

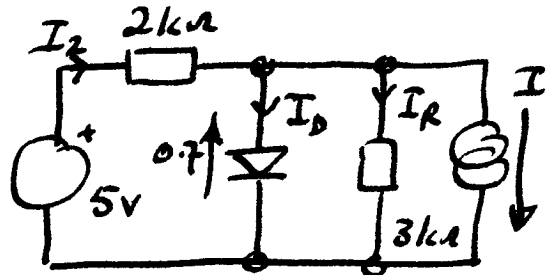

Summing current at diode anode node ...

$$I_2 = I_D + I_R + I$$

$$\text{or } \frac{5 - 0.7}{2k\Omega} = I_D + \frac{0.7}{3k\Omega} + I.$$

and if $I_D = 0$,

$$\frac{4.3}{2k\Omega} - \frac{0.7}{3k\Omega} = I = \underline{\underline{1.92mA}}$$

Q3 (a) -

(b) - assume diodes are non conducting...

V_{A1} = 20mA × 2kΩ = 40V.

V_{C2} = 20mA × 4kΩ = 80V


V_{A2} = 10mA × 10kΩ = 100V

V_{C1} = 10mA × 11kΩ = 110V.

∴ V_{A1} - V_{C1} = 40 - 110 = -70V.

V_{A2} - V_{C2} = 100 - 80 = +20V

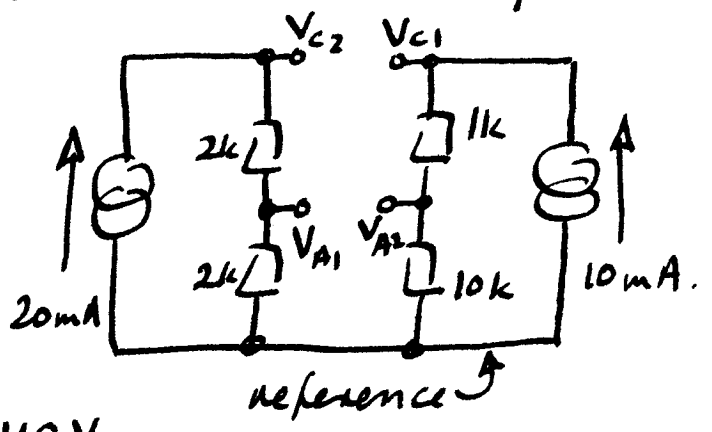∴ diode 1 is not conducting.
diode 2 is conducting.




The circuit must now be re-examined with D₁ not conducting and D₂ conducting to find the forward current through D₂ and to check that D₁'s state is not affected by the wrong assumption about D₂.

- using loops ...

I₂ = -20mA

I₁ = 10mA.

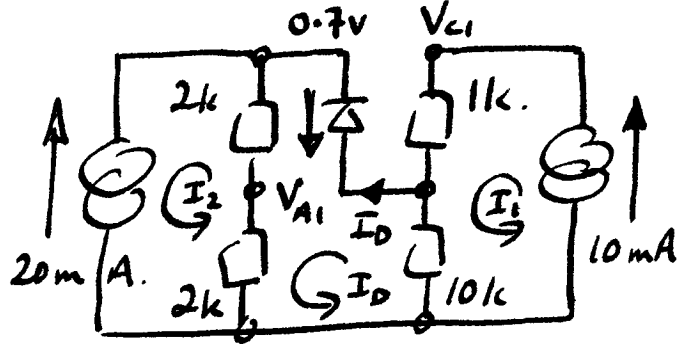

(I_D - I₂) 2k + (I_D - I₁) 10k + (I_D - I₂) 2k + 0.7 = 0.

I_D [2k + 10k + 2k] + 0.7 + 40V - 100V + 40V = 0.

I_D = $\frac{19.3}{14k\Omega} = \underline{\underline{1.38mA}}$

V_{A1} = 2k(I_D - I₂) = 2k(1.38 + 20)mA = 42.8V


V_{C1} = 10mA × 11k - (I_D - 10mA) 10k = 96.2V

∴ D₁ still non - conducting.

Q4 (a) - let the voltage across the diode be 0.7V.

$$I_1 = 10 \text{ mA}$$

$$I_D = I_2 - I_3.$$

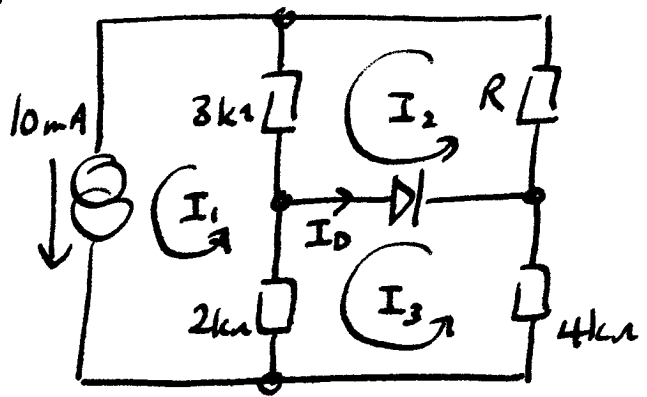

$$(I_2 - I_1) 3k\Omega + 0.7 + I_2 R = 0 \quad [I_2 \text{ loop}]$$

or $I_2 (3k\Omega + R) = 30 - 0.7 = 29.3.$

$$(I_3 - I_1) 2k\Omega - 0.7 + I_3 4k\Omega = 0.$$

or $I_3 = \frac{20.7}{6k\Omega} = 3.45 \text{ mA}.$

$$I_D = 0 = \frac{29.3}{3k\Omega + R} - 3.45 \text{ mA}.$$


$$\text{or } R = \frac{29.3 - 3.45 \text{ mA} \times 3k\Omega}{3.45 \text{ mA}}.$$

$$= \frac{29.3}{3.45 \text{ mA}} - 3k\Omega = \underline{\underline{5.49k\Omega}}.$$

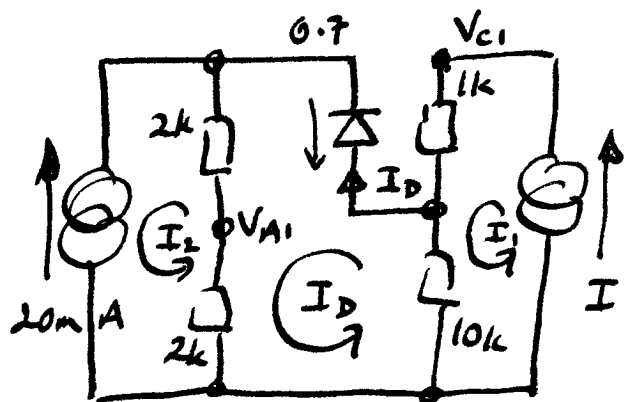(b) $I_2 = -20 \text{ mA}$

$$I_1 = I$$

$$(I_D - I_1) 10k + 0.7 + (I_D - I_2) 4k = 0.$$




or $I_D 14k - 10k I + 80 + 0.7 = 0.$

if $I_D = 0$, $I = \frac{80.7}{10k} = \underline{\underline{8.07 \text{ mA}}}$

$[V_{AI} = 40V, V_{CI} = 88.7V \text{ so } D_1 \text{ remains in a non-conducting state.}]$

(c) - There is 0.7 across D_1 and D_2 and the condition sought is $I_D = 0$.

$$I_R = 0.7 / 2k\Omega$$

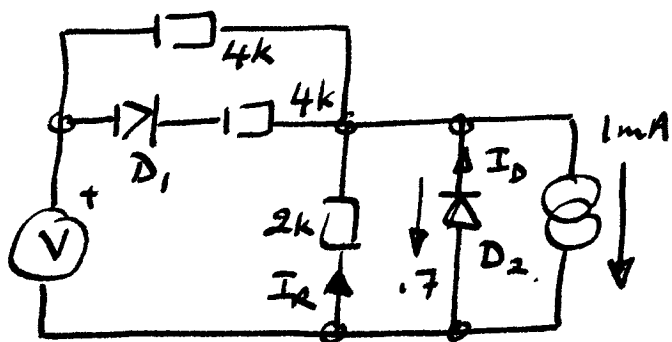

Summing currents at D_2 cathode node....

$$I_D + I_R - 1mA + \frac{(V - (-0.7))}{4k\Omega} + \frac{(V - 0.7 - (-0.7))}{4k\Omega} = 0$$

$$\text{or } I_D + 0.7 / 2k\Omega - 1mA + \frac{2V}{4k\Omega} + \frac{0.7}{4k\Omega} = 0$$

$$\text{if } I_D = 0, \quad \frac{2V}{4k\Omega} = 1mA - \frac{0.7}{2k\Omega} - \frac{0.7}{4k\Omega}$$

$$= 475\mu A$$

$$\therefore V = \frac{475\mu A \times 4k\Omega}{2}$$

$$= \underline{\underline{0.95V}}$$

$$\text{with } V = 0.95, \quad I_{D1} = \frac{V - 0.7 - (-0.7)}{4k\Omega}$$

$$= \frac{0.95}{4k\Omega} = \underline{\underline{237.5\mu A}}$$

so D_1 is still in a conducting state.