

EEE103/EEE121/EEE141 Problem Solutions

Transistors as Switches and Amplifiers


Q1 It is important to ensure that a transistor switch is driven on and off properly in order to minimise power dissipation within the switch. When on, one wants a small voltage across the switch so that $I_{ON}V_{ON}$ is small and when off one wants a small current through the switch (ideally zero) so that $I_{OFF}V_{OFF}$ is small. If the switch is only half switched on, the VI product dissipated within it is likely to destroy it.

$$(i) I_{ON} = \frac{50V}{40\Omega} = \underline{\underline{1.25A}}$$

(assumes V_{CESAT} negligible).

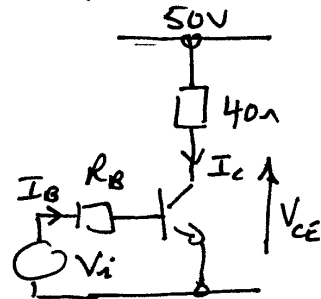(ii) Worst case I_B (ie largest I_B) occurs for smallest h_{FE} .

$$\begin{aligned} \therefore I_{Bmax} &= \frac{I_{CON}}{h_{FEMIN}} \\ &= \frac{1.25A}{70} = \underline{\underline{17.86mA}} \end{aligned}$$



(iii) R_B must be small enough to provide the on state I_B required by a transistor with the lowest h_{FE} ... ie, the answer to part (ii).

$$\begin{aligned} \therefore R_{Bmax} &= \frac{10 - 0.7}{17.86mA} \left[= \frac{V_i - V_{BE}}{I_{Bmax}} \right] \\ &= \underline{\underline{521\Omega}} \end{aligned}$$

(iv) Power lost in transistor during "on" state is

$$\begin{aligned} P_D &= I_{CON} \cdot V_{CESAT} = 1.25A \times 0.25V \\ &= \underline{\underline{313mW}} \end{aligned}$$

(2)

Q2 In their "on" state, MOSFETs look like a resistance of $r_{DS(on)}$ so the power dissipation is $I_{D(on)}^2 r_{DS(on)}$.

$$= 1.25^2 \times 0.25 \Omega = \underline{390 \text{ mW}}.$$

[This assumes that the "on" resistance of the MOSFET does not significantly alter $I_{D(on)}$ i.e., that $r_{DS(on)} \ll R_L$; clearly true here]

Since the MOSFETs dissipate more energy as heat, they are less attractive than the BJT.

Q3 (i) If S has been on for a long time..

$$(i) E = \frac{1}{2} L I^2 = \frac{1}{2} \times 0.1 \times 1.25 \text{ A}^2 = \underline{78 \text{ mJ}}.$$

(ii) D and R provide a path by which the inductor can maintain current continuity when the switch switches off. They do it in a way that defines the maximum off state voltage across the switch.

(iii) $I_D = I_{con} = \underline{1.25 \text{ A}}$ immediately after the switch opens.

(iv) The decay time constant is $L/R_L = \frac{100 \text{ mH}}{40 \Omega} = \underline{2.5 \text{ ms}}$.

(v) I_D will create a voltage across R with its positive end at D's cathode. This voltage, $I_D R$, will add to the 50V supply to give the switch off-state voltage.

If S can cope with 200V, $50 + I_{Dmax} R = 200$

$$\text{or } R = \frac{200 - 50}{1.25} = \frac{150}{1.25} = \underline{120 \Omega}.$$

(vi) If the switch switches 50 times per second, Energy loss per second, which equals power is


$$P = 78 \text{ mJ} \times 50 = 3.9 \text{ W.}$$

This power is shared between R and the 40Ω internal resistance of the load and since the same I_D flows through both, power is proportional to R .

$$\begin{aligned} \text{Thus } P_R &= 3.9 \text{ W} \times \frac{R}{40+R} = 3.9 \times \frac{100}{140} \\ &= \underline{2.8 \text{ W}}. \end{aligned}$$

[Note that the 40Ω part of the load will also dissipate energy in the "on" state - in this case at a rate of 62.5 W - so the energy stored in L contributes only a small increment to this for the conditions of the question]

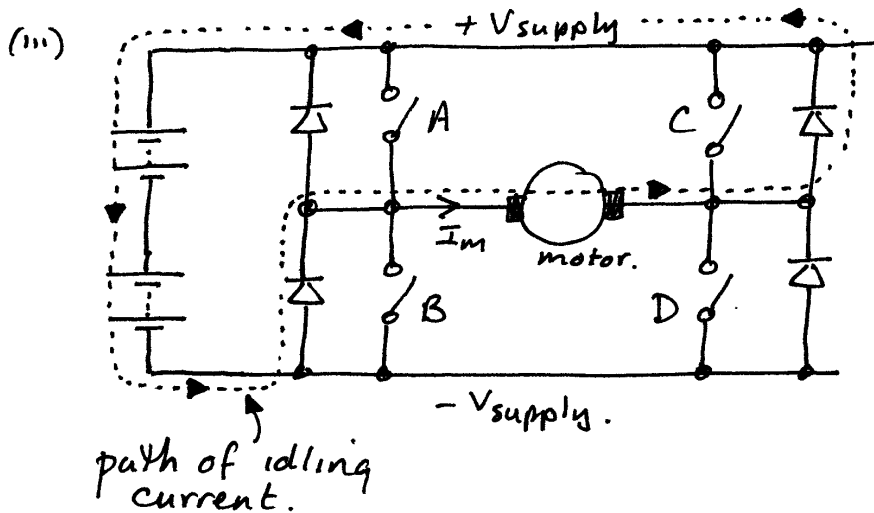
- Q4 (i) switches A and D will cause clockwise motion when on.
- (ii) switches C and B will cause anti-clockwise motion when on.



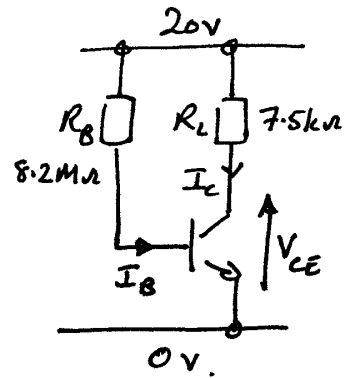(4)

$$\text{Q5 (i) } I_B = \frac{20 - V_{BE}}{8.2 \text{ M}\Omega}$$

$$= \frac{19.3}{8.2 \text{ M}\Omega} = \underline{2.35 \mu\text{A}}$$



$$\text{(ii) } I_{C \text{ max}} = I_B h_{FE \text{ max}}$$

$$= 2.35 \mu\text{A} \times 850$$

$$= 2 \text{ mA.}$$

$$I_{C \text{ min}} = I_B h_{FE \text{ min}} = 2.35 \mu\text{A} \times 100 = 235 \mu\text{A.}$$

$$V_{CE} = 20 - I_C R_L$$

$$= 20 - 2 \text{ mA} \times 7.5 \text{ k}\Omega = \underline{5 \text{ V}} \text{ for } h_{FE} = 850$$

$$= 20 - 235 \mu\text{A} \times 7.5 \text{ k}\Omega = \underline{18.2 \text{ V}} \text{ for } h_{FE} = 100$$

(iii) The cct is a poor bias circuit because it fails to control I_C ; instead it controls I_B .

(iv) From the cct, $V_{CE} = V_{CC} - I_C R_L$, and using $h_{FE} = I_C / I_B$ this can be written

$$V_{CE} = V_{CC} - h_{FE} I_B R_L. \quad \text{--- (1)}$$

The normalised change in h_{FE} with temp is 0.5%

$$\text{ie } \frac{1}{h_{FE}} \cdot \frac{dh_{FE}}{dT} = \frac{0.5}{100} \quad \text{--- (2)}$$

[If you have trouble with this, put it in terms of money. If someone was to pay you 0.5% of \$450 per week, how much would you get per week?]

$$\frac{dV_{CE}}{dT} = \frac{dV_{CE}}{dh_{FE}} \cdot \frac{dh_{FE}}{dT} \quad \text{--- by differentiating (1)}$$

$$= -I_B R_L \cdot \frac{0.5 h_{FE}}{100} \quad \text{--- by rearranging (2)}$$

$$= -2.35 \mu\text{A} \times 7.5 \text{ k}\Omega \times \frac{0.5 \times 450}{100}$$

$$= \underline{\underline{-40 \text{ mV}/^\circ\text{C}}}$$


5

$$\begin{aligned} \text{Q6 (i)} \quad V_B &= 20 \frac{R_2}{R_1 + R_2} \\ &= \frac{20 \cdot 39 \text{ k}\Omega}{199 \text{ k}\Omega} = \underline{3.92 \text{ V}} \end{aligned}$$

$$\begin{aligned} V_E &= V_B - V_{BE} \\ &= 3.92 - 0.7 = \underline{3.22 \text{ V}} \end{aligned}$$

$$I_E \approx I_C = \frac{3.22 \text{ V}}{R_E} = \underline{3.22 \text{ mA}}$$

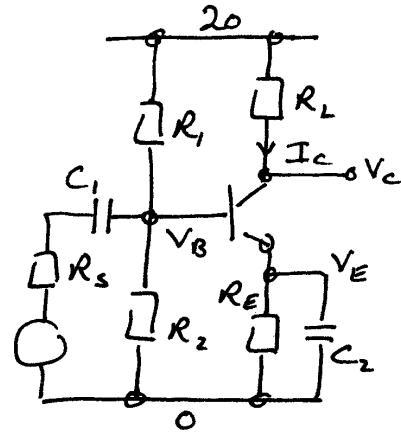
$$\begin{aligned} V_C &= V_{CC} - I_C R_L = 20 - 3.22 \times 2.4 \text{ k}\Omega \times 10^{-3} \\ &= 20 - 7.73 = \underline{12.3 \text{ V}} \end{aligned}$$



$$\text{(ii)} \quad g_m = \frac{e I_C}{kT} = \frac{3.22 \text{ mA}}{1026 \text{ V}} = \underline{0.124 \text{ A/V}}$$

$$r_{be} = \beta / g_m = \frac{500}{0.124} = \underline{4.04 \text{ k}\Omega}$$

(iii)

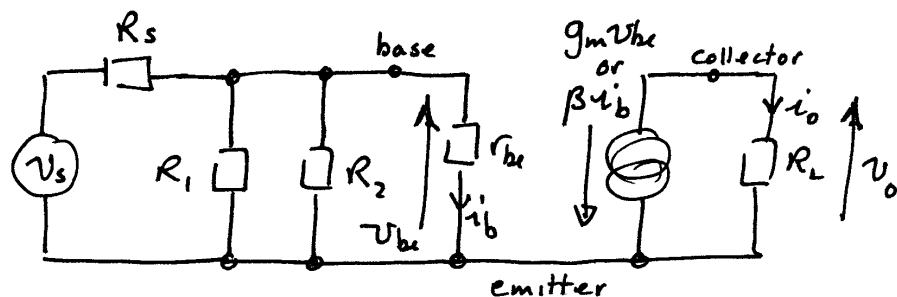

$$\text{(iv)} \quad \frac{V_o}{V_s} = \frac{V_o}{V_{be}} \times \frac{V_{be}}{V_s}$$

$$\frac{V_o}{V_{be}} = -g_m R_L \quad (\text{since } i_o = -g_m V_{be} R_L)$$

$$\frac{V_{be}}{V_s} = \frac{R_1 \parallel R_2 \parallel r_{be}}{R_s + R_1 \parallel R_2 \parallel r_{be}} = \frac{3.58 \text{ k}\Omega}{10 \text{ k}\Omega + 3.58 \text{ k}\Omega} = 0.263$$

$$\therefore \frac{V_o}{V_s} = -g_m R_L \times 0.263 = \underline{78.3}$$

6


(v) follow the same general process as in Q5 pt (iv). Here the feedback makes the equations more cumbersome

First replace $R_1 + R_2$ by a Thevenin equiv (not essential but makes it a bit easier).

$$V_B = I_B R_B' + 0.7 + I_E R_E$$

$$\text{but } I_E = I_B + I_C$$
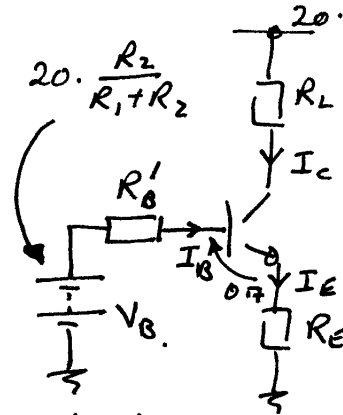
$$\begin{aligned} \therefore V_B &= I_B R_B' + 0.7 + I_B R_E + I_C R_E \\ &= I_B (R_B' + R_E) + 0.7 + I_C R_E \end{aligned}$$



now I_C is the variable of interest in the question so eliminate I_B using $I_B = \frac{I_C}{h_{FE}}$

$$\therefore V_B = \frac{I_C}{h_{FE}} (R_B' + R_E) + 0.7 + I_C R_E$$

$$\text{or } I_C = \frac{(V_B - 0.7) h_{FE}}{R_B' + R_E + h_{FE} R_E} = \frac{3.22 h_{FE}}{R_B' + R_E + h_{FE} R_E} \quad \text{--- ①}$$

[one could say here $R_E + h_{FE} R_E \approx h_{FE} R_E$ if $h_{FE} \gg 1$]

As in Q5 pt (iv)

$$\frac{dI_C}{dT} = \frac{dI_C}{dh_{FE}} \times \frac{dh_{FE}}{dT} \quad \dots \text{by differentiating } \text{①}$$

\dots from ② in Spt (iv).

$$\frac{dI_C}{dh_{FE}} = \frac{(R_B' + R_E + h_{FE} R_E) \cdot 3.22 - R_E \cdot 3.22 h_{FE}}{(R_B' + R_E + h_{FE} R_E)^2}$$

$$\text{note from ① that } (R_B' + R_E + h_{FE} R_E)^2 = \left(\frac{3.22 h_{FE}}{I_C} \right)^2$$

$$\begin{aligned} \text{so } \frac{dI_C}{dh_{FE}} &= \frac{3.22 (R_B' + R_E) I_C^2}{(3.22 h_{FE})^2} \\ &= \frac{3.22 (R_B' + R_E) 3.22^2 \times 10^{-6}}{3.22^2 \cdot 450^2} \end{aligned}$$

$$\frac{dI_C}{dT} = \frac{3.22 (R_B' + R_E) \times 10^{-6}}{450^2} \cdot \frac{450 \times 0.5}{100} = \underline{\underline{1.16 \mu A / ^\circ C}}$$

[This gives a V_C dependency of $-2.78 \text{ mV / } ^\circ \text{C}$]

(7)

Q7 (i) you need to find two equations with I_F and I_C as unknowns...

$$24 = (I_C + I_F)R_L + I_F(R_1 + R_2) + I_F R_3$$

$$\text{or } 24 = I_C R_L + I_F(R_L + R_1 + R_2 + R_3) \quad \text{--- (1)}$$

$$\text{and } I_F R_3 = 0.7 + I_C R_E \quad \text{--- (2)}$$

(This assumes $I_E \approx I_C$).

eliminating I_F from (1) + (2) ...

$$24 = I_C R_L + \frac{0.7 + I_C R_E}{R_3} (R_L + R_1 + R_2 + R_3)$$

$$\text{or } 24 = I_C \times 10\text{ k}\Omega + 0.7 \times 4.467 + I_C \times 2.7 \times 10^3 \times 4.467$$

$$= I_C (10\text{ k}\Omega + 12.06\text{ k}\Omega) + 3.13$$

$$\text{or } I_C = \frac{20.87}{22.06\text{ k}\Omega} = \underline{\underline{946\ \mu\text{A}}}$$

$$\therefore \text{from (2), } I_F = \underline{\underline{108\ \mu\text{A}}}$$

$$V_E = I_C R_E = \underline{\underline{2.55\ \text{V}}}$$


$$V_C = 24 - (I_C + I_F)R_L = 24 - 1.054\text{ mA} \times 10\text{ k}$$

$$= \underline{\underline{13.5\ \text{V}}}$$

$$(ii) \quad g_m = \frac{e I_C}{kT} = \frac{946 \times 10^{-6}}{0.026} = \underline{\underline{36.4\ \text{mA/V}}} \quad (0.0364\ \text{A/V})$$

$$r_{be} = \beta / g_m = \frac{500}{0.0364} = \underline{\underline{13.7\ \text{k}\Omega}}$$

(iii)

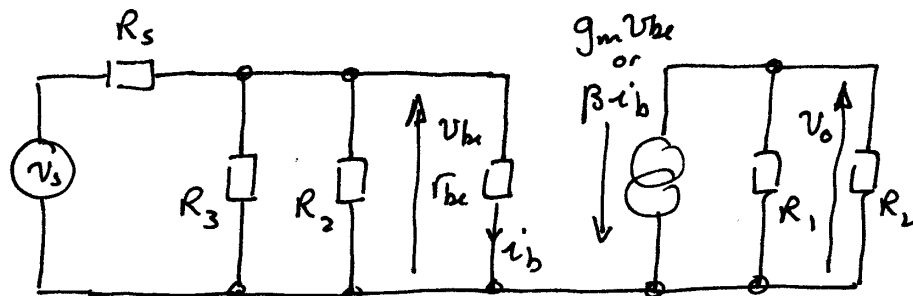

(iv) if $R_s = 0$, $v_s = v_{be}$ and gain is

$$\frac{v_o}{v_s} = \frac{v_o}{v_{be}} = -g_m R_L \parallel R_F = \underline{\underline{-300}}$$


if $R_s = 10 \text{ k}\Omega$

$$\frac{v_o}{v_s} = \frac{v_o}{v_{be}} \times \frac{v_{be}}{v_s}$$

$$\frac{v_{be}}{v_s} = \frac{R_3 \parallel R_2 \parallel r_{be}}{R_s + R_3 \parallel R_2 \parallel r_{be}} = \frac{7.84 \text{ k}\Omega}{17.84 \text{ k}\Omega} = 0.439$$

$$\therefore \frac{v_o}{v_s} = -300 \times 0.439 = \underline{\underline{-132}}$$

(v) if C_3 removed the cct changes to

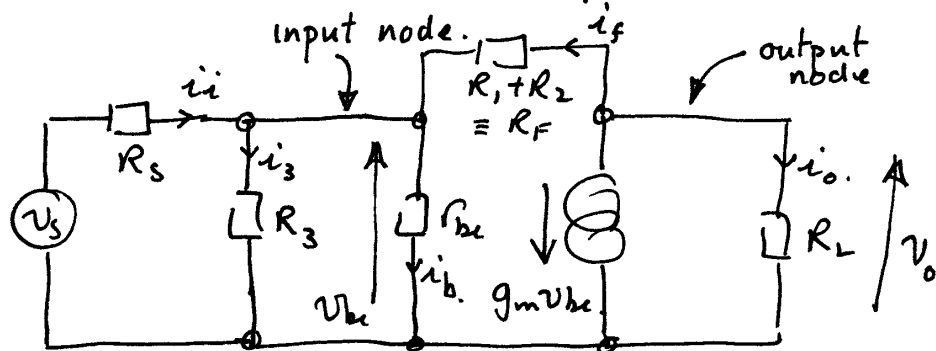

Sum currents at output node

$$i_f + i_o + g_m v_{be} = 0$$

$$\text{or } \frac{v_o - v_{be}}{R_F} + \frac{v_o}{R_L} + g_m v_{be} = 0 \quad \text{--- (1)}$$

Sum currents at input node

$$i_i + i_f = i_3 + i_b$$

$$\text{or } \frac{v_s - v_{be}}{R_s} + \frac{v_o - v_{be}}{R_F} = \frac{v_{be}}{R_3} + \frac{v_{be}}{r_{be}} \quad \text{--- (2)}$$

v_{be} can be eliminated from (1) + (2) to give

(9)

$$\frac{v_o}{v_s} = \frac{1/R_s}{\left[\frac{R_L + R_F}{R_L(1 - g_m R_F)} \left(\frac{1}{R_s} + \frac{1}{R_F} + \frac{1}{R_3} + \frac{1}{r_{be}} \right) - \frac{1}{R_F} \right]}$$

$$= \underline{\underline{-8.85}}$$

The big reduction of gain here occurs because there is now feedback between collector + base (via R_F) that operates on the signal.