

# Op-Amp Anatomy

## Basic op-amp circuit

### Introduction

Figure 1 shows a circuit that contains the basic elements of an op-amp. The elements are the simplest circuits that will perform the required basic function and so are not optimised to give

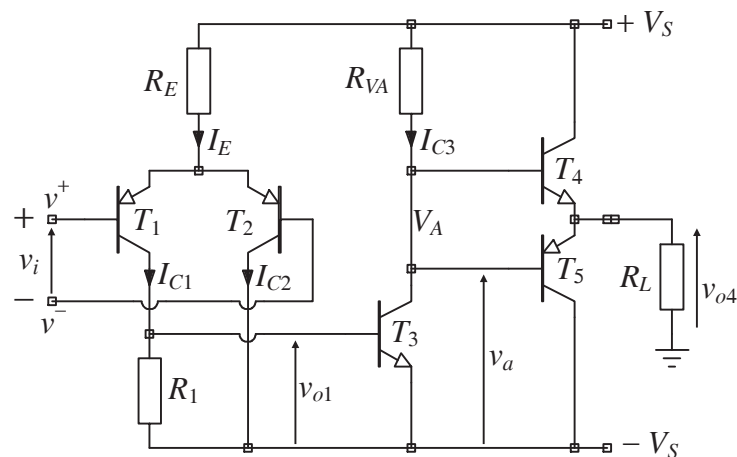


Figure 1

a good op-amp performance. The treatment that follows looks first at this basic circuit from a dc condition point of view and then explores the way the circuit responds to signals which can be regarded as small changes superimposed on the dc conditions. The study of the response of the circuit to small changes in dc conditions is called "small-signal" (ss) analysis. In principle ss analysis yields results that are frequency dependent but here we assume that frequencies are sufficiently low that no reactive effects are significant.

After identifying the problems associated with the basic circuit of figure 1, refinements are added to the circuit that increase complexity but also make the design perform more effectively as an op-amp.

### Evaluating dc conditions

There are some key ideas about op-amps that must be borne in mind when working out dc conditions:

- No op-amp will work properly without feedback. The feedback controls the gain of the circuit but also performs a crucial role in defining the circuit dc conditions. The feedback will alter the dc value of  $v_i$  in order to achieve the internal voltage drops required for proper operation. This means that if  $v_o = 0$ ,  $v_i$  will be at the value it needs to have in order to make  $v_o = 0$  and in a good op-amp this value will be very small.
- The "differential input voltage",  $v_i$  in figure 1, is the difference  $v^+ - v^-$ .

- The "common mode input voltage" is the average of  $v^+$  and  $v^-$ , ie,  $(v^+ + v^-)/2$

In the circuit of figure 1 the common mode input voltage will affect the internal amplifier currents so the assumption will be made here that  $v^+ \approx v^- \approx 0$ . It is not difficult to apply the process below to a case where common mode voltage is non-zero. Whatever the common mode voltage,  $v^+ \approx v^-$  will be a valid assumption.

If  $v^+ \approx v^- \approx 0$ ,  $V_{E1}$  and  $V_{E2} \approx 0.7$  so  $I_E \approx (V_S - 0.7)/R_E$ .  $I_E$  splits between  $T_1$  and  $T_2$  to form  $I_{C1}$  and  $I_{C2}$ .  $I_{C1}$  has two functions; it must create a voltage drop of 0.7 V across  $R_1$  in order to bias  $T_3$  into conduction and it must provide the necessary base current for  $T_3$ . This means that  $I_{C1}$  will be  $0.7/R_1 + I_{C3}/h_{FE3}$ . The value of  $I_{C3}$  varies with  $V_A$  and hence with  $V_O$  but assuming  $V_A = 0$ ,  $I_{C3} = V_S/R_{VA}$ .  $I_{C2}$  is returned directly to the negative supply. In the case where  $v^+ \approx v^- \neq 0$ , there is a common mode input voltage,  $v_{cm}$ , and  $I_E \approx (V_S - v_{cm})/R_E$ . The rest of the process is as just described.

The biggest problem with this simple circuit is that a small value of  $I_E$  is desirable to give the op-amp a high input resistance and for keeping noise to a minimum. It is desirable to have an equal split of  $I_E$  between  $I_{C1}$  and  $I_{C2}$  in order to minimise input stage imbalance which causes offset problems.  $I_{C1}$  supplies both  $I_{b3}$  and  $I_{R1}$  and although  $I_{R1}$  is reasonably predictable,  $I_{b3}$  depends upon  $h_{FE3}$  which may vary from one op-amp to another. This variation can lead to relatively large imbalances between  $I_{C1}$  and  $I_{C2}$ . A remedy for this problem will be described later in the "refinements" section.

## Evaluating signal related behaviour


The behaviour of the circuit towards signals is evaluated with the help of ss models of the circuit. Since even the simple circuit of figure 1 contains several transistors it is most useful to look at the behaviour of each stage in turn. The objective of the analysis is to identify which circuit components are important players in key performance factors such as voltage gain. We will start the consideration of signal related effects by reviewing the ss behaviour of standard transistor connections.

## Small signal review

### The common emitter (CE) connection

The common emitter connection is a connection that gives a large voltage gain. It can be configured using either n-p-n or p-n-p transistors as shown in figure 2. Both the n-p-n and p-n-p versions have the same small signal equivalent circuit shown in figure 3. The resistors  $R_S$  are the Thevenin equivalent resistance feeding the base and it is assumed that the bias circuit is included within  $R_S$ .  $R_L$  represents the total resistance between the collector node and signal ground - it is often called the "collector load resistance".

The small signal circuit of a CE amplifier is shown in figure 3.  $R_L$  usually con-

 

**Figure 2**

An n-p-n (left) and a p-n-p (right) common emitter circuit. Note the difference in power supply polarity in the two cases.

sists of three parallel components; the collector load required locally for biasing, the effective collector-emitter resistance,  $r_{ce}$ , of the transistor and the input resistance of the external load that is being driven by the amplifier.  $r_{ce}$  is often sufficiently large to make a negligible difference to this parallel combination and under such circumstances it can be ignored.

The absence of feedback in the circuit makes it straightforward to find the circuit gain.

$$\text{At the output, } v_o = i_o R_L = -g_m v_{be} R_L \text{ since } i_o = -g_m v_{be} \quad (1)$$

$$\text{At the input, } v_{be} = v_s \frac{r_{be}}{R_S + r_{be}} \quad (2)$$

$$\text{using (2) to substitute for } v_{be} \text{ in (1) gives } \frac{v_o}{v_s} = -g_m R_L \frac{r_{be}}{R_S + r_{be}} \quad (3)$$

The important conclusions are

- the gain is inverting (the "-" sign tells us this).
- gain is proportional to  $g_m$  (so large  $g_m$ s are attractive).
- gain is proportional to  $R_L$  (so large  $R_L$ s are attractive).
- $r_{be} \gg R_S$  must be satisfied to avoid significant input circuit attenuation.

The other parameter of interest for this transistor connection is its input resistance,  $r_i$ , looking into the transistor base terminal - that is, the effective resistance between the base terminal and ground. A quick glance at figure 3 will reveal that

$$r_i = r_{be}. \quad (4)$$


### The common emitter connection with emitter degeneration

Sometimes CE circuits have a small value of resistance - typically 10s of  $\Omega$  to low  $k\Omega$  - between the emitter terminal and ground as shown in figure 4. This resistance is called an "emitter degeneration" resistance. The effect that emitter degeneration has on the shape of the small signal equivalent circuit is simply to add a resistor  $R_E$  between the emitter node and ground as shown in figure 5. Unfortunately this addition significantly complicates the small signal analysis, especially if  $r_{ce}$  is included in the analysis, because  $R_E$  couples the output circuit to the input circuit. In the analysis that follows we will assume that  $r_{ce}$  has a negligible effect.

Summing currents at the emitter node in figure 5


$$i_b + g_m v_{be} = i_e \text{ or } \frac{v_{be}}{r_{be}} + g_m v_{be} = \frac{v_e}{R_E} \quad (5)$$

we need to express  $v_e$  in terms of  $v_s$ ,  $v_o$ ,  $v_{be}$  and the circuit components. Rearranging (5) gives

 

**Figure 3**

The small signal representation of both the circuits in figure 2

 

**Figure 4**

A common emitter amplifier with emitter degeneration

$$v_e = v_{be} R_E \left( \frac{1}{r_{be}} + g_m \right) \approx v_{be} R_E g_m \quad (6)$$

the simplification is justified since  $1/r_{be} = g_m/\beta$  and  $\beta \gg 1$

A second equation can be obtained by summing voltages around the input loop

$$v_s = i_b R_S + v_{be} + v_e$$

Recognising that  $i_b = v_{be}/r_{be}$  and using (6) for  $v_e$  this becomes

$$v_s = v_{be} \left( 1 + \frac{R_S}{r_{be}} + g_m R_E \right) \quad (7)$$

At the output side of the circuit,  $v_o = i_o R_L$  and  $i_o = -g_m v_{be}$ . Thus, using (7)

$$v_o = -g_m R_L v_{be} = - \frac{g_m R_L v_s}{\left( 1 + \frac{R_S}{r_{be}} + g_m R_E \right)}$$

$$\text{and } \frac{v_o}{v_s} = - \frac{g_m R_L}{\left( 1 + \frac{R_S}{r_{be}} + g_m R_E \right)} = - \frac{R_L}{\left( r_e + \frac{R_S}{\beta} + R_E \right)} \text{ where } r_e = 1/g_m. \quad (8)$$

The important conclusions are

- the gain is inverting
- the gain is proportional to  $R_L$
- $R_E$  reduces the gain
- If  $R_E \gg 1/g_m$  and  $R_S/\beta$ , gain  $\approx -R_L/R_E$

[Note that although  $R_E$  is quite commonly found in low frequency amplifiers, for high frequency (10s MHz or higher) amplifier circuits,  $R_E$  is almost always undesirable. Indeed one of the big design challenges in RF circuit design is to ensure a low impedance connection between signal ground and transistor emitter. Any impedance in the  $R_E$  position interacts with the frequency dependent aspects of the transistor's equivalent circuit in such a way as to encourage instability in the amplifier. Instability in this context means a tendency to oscillate - ie produce an output with no input - at a high frequency, always an undesirable characteristic in an amplifier.]

The presence of  $R_E$  also affects the input resistance of the circuit looking into the transistor base terminal. The input resistance is defined by  $v_b/i_b$  where  $v_b$  is the signal voltage at the base terminal with respect to signal ground.


Summing voltages and using the unsimplified form of (6) to express  $v_e$  in terms of  $v_{be}$

$$v_b = v_{be} + v_e = v_{be} + v_{be} R_E \left( \frac{1}{r_{be}} + g_m \right) = v_{be} \left( 1 + R_E \left( \frac{1}{r_{be}} + g_m \right) \right)$$

and since  $v_{be} = i_b r_{be}$  and  $g_m r_{be} = \beta$ , the input resistance can be written

$$r_i = \frac{v_b}{i_b} = r_{be} + (\beta + 1)R_E \quad (9)$$

- The input resistance has been increased by an amount  $(1 + \beta)R_E$  compared to the non  $R_E$  case of (4). If  $\beta = 300$ , say, a typical value for an amplifier transistor, a small  $R_E$  can have a significant effect on input resistance.

 

**Figure 5**

CE circuit with emitter degeneration

## The "common collector" or "emitter follower" connection

The common collector circuit is one of a class of circuits known as voltage follower circuits. The name arises because the output voltage follows closely the input voltage; the gain is very close to but always less than unity. The common collector circuit can be realised using n-p-n or p-n-p transistors; the n-p-n version is shown in figure 6. As with figures 2 and 4, it is assumed that the effective bias circuit resistance is included in  $R_S$ . Notice the similarity to the common emitter with emitter degeneration circuit of figure 4 - the only difference between that and figure 6 is that in figure 6 there is no  $R_L$  and the output is taken across  $R_E$ .

The small signal equivalent circuit of the emitter follower is shown in figure 7 which has similarities with figure 5. The analysis is very similar to that associated with figure 5 except that  $v_e$  has become  $v_o$  and does not now need to be eliminated. The analysis begins by summing currents at the emitter node, the same process that led to (5) and (6). (6) is repeated below with  $v_e$  replaced by its name in this analysis,  $v_o$ .

$$v_o = v_{be} R_E \left( \frac{1}{r_{be}} + g_m \right) \approx v_{be} R_E g_m \quad (10)$$

A second equation relating  $v_{be}$ ,  $v_s$  and  $v_o$  is obtained by summing voltages around the input loop

$$v_s = i_b R_S + v_{be} + v_o = v_{be} \left( 1 + \frac{R_S}{r_{be}} \right) + v_o \quad (11)$$

and using the approximate result of (10) to eliminate  $v_{be}$  from (11) gives

$$\frac{v_o}{v_s} = \frac{r_{be} g_m R_E}{\left( r_{be} g_m R_E + R_S + r_{be} \right)} = \frac{R_E}{\left( r_e + \frac{R_S}{\beta} + R_E \right)} \quad \text{where } r_e = 1/g_m. \quad (12)$$


The important conclusions are

- the gain is non-inverting
- the gain is very close to unity if  $R_E \gg R_S/\beta$  and  $1/g_m$ , conditions that are usually satisfied.

The input resistance looking into the base terminal is as described for the common emitter with emitter degeneration in the analysis leading to (9). The result is repeated here


$$r_i = \frac{v_b}{i_b} = r_{be} + (\beta + 1)R_E \quad (13)$$

- the input resistance is dominated by the  $(\beta + 1)R_E$  term.

 

**Figure 6**

*The emitter follower circuit*

 

**Figure 7**

*Small signal equivalent circuit of an emitter follower*

## The common base connection

Although sometimes used on its own, the common base connection is most commonly used in combination with other circuits - ie, as part of a multi transistor sub-circuit block. The circuit of a common base connected n-p-n device is shown in figure 8 and once again there is a p-n-p version of this circuit. It is assumed that any biasing resistances are included in  $R_S$ . Since  $I_C$  is large compared to  $I_B$  and  $I_E = I_C + I_B$ , the approximation  $I_C \approx I_B$  is usually valid.

The ss equivalent circuit is shown in figure 9. The effects of  $r_{ce}$  are neglected. The analytical process follows a similar pattern to the previous examples although the results are different. Start by summing currents at the emitter node,

$$i_s + i_b + g_m v_{be} = 0$$

$$\text{or } \frac{v_s - v_e}{R_S} + \frac{v_{be}}{r_{be}} + g_m v_{be} = 0 \quad (14)$$

Note that  $v_e + v_{be} = 0$  so  $v_e = -v_{be}$  and this allows (14) to be rearranged to give  $v_{be}$  in terms of  $v_s$ ,

$$v_{be} = - \frac{v_s}{R_S \left( \frac{1}{R_S} + \frac{1}{r_{be}} + g_m \right)} \approx - \frac{v_s}{1 + g_m R_S} \quad (15)$$

since  $1/r_{be} = g_m/\beta$  and  $\beta \gg 1$ .

At the output side

$$v_o = i_o R_L = -g_m v_{be} R_L \text{ and combining this with (15) to eliminate } v_{be} \text{ gives}$$

$$\frac{v_o}{v_s} = \frac{g_m R_L}{1 + g_m R_S} = \frac{R_L}{r_e + R_S} \text{ where } r_e = 1/g_m. \quad (16)$$


The important conclusions are

- the gain is non-inverting.
- gain is proportional to  $R_L$ .
- If  $R_S \gg r_e$  the gain is controlled by the ratio  $R_L/R_S$ .

The input resistance looking into the emitter of the transistor is given by


$$r_i = \frac{v_e}{i_e} = \frac{v_e}{\frac{-v_{be}}{r_{be}} - g_m v_{be}} \text{ but since } v_e = -v_{be} \text{ and } g_m \gg 1/r_{be} \text{ this reduces to}$$

$$r_i \approx \frac{1}{g_m} = r_e, \text{ a relatively low value (10s to 100s of Ohms).} \quad (17)$$

 

**Figure 8**

A common base circuit. The bias circuit is part of the thevenin resistance  $R_S$ .

 

**Figure 9**

The small signal model of the circuit of figure 8. Note that  $r_{ce}$  is omitted from the model

## Back to the simple op-amp of figure 1 . . . .

The parameters that we will work out here are overall gain and input resistance. The input resistance of the op-amp is essentially the first stage input resistance. The voltage gain of the op-amp is the voltage gain of the differential input stage multiplied by the voltage gain of the voltage amplification stage multiplied by the voltage gain of the output stage.

### The input stage

The input stage circuitry is shown in figure 10. We must consider the effects of three transistors.  $T_1$  and  $T_2$  are the input differential pair and must be considered together and  $T_3$  must be considered because its input resistance forms part of  $T_1$ 's collector load resistance. If the input signal is regarded as  $v_{bT1}$  with respect to  $v_{bT2}$  (ie,  $v_{bT2}$  is taken as a signal ground),  $T_2$  looks like a common base connection as far as  $T_1$  is concerned and can be represented by its common base input resistance given by (17) as  $r_{e2}$  ( $= 1/g_{m2}$ ). The collector current of  $T_1$  sees two resistors in parallel,  $R_1$  and the input resistance of  $T_3$ .  $T_3$  is a common emitter connection and its input resistance is given by (4) as  $r_{be3}$ .

A small signal equivalent circuit that embodies these representations of  $T_2$  and  $T_3$  is shown in figure 11. The circuit of figure 11 is the same as that of figure 5 with the exceptions that  $R_S = 0$  and  $R_E$  and  $R_L$  become the parallel combinations  $R_E/r_{e2}$  and  $R_1/r_{be3}$  respectively. Since in figure 11  $R_E \gg r_{e2}$ , the parallel combination  $R_E/r_{e2} \approx r_{e2}$ . Including these variable changes in (8), the gain expression for figure 5, the voltage gain of the circuit of figure 11 is

$$\frac{v_{o1}}{v_i} \approx - \frac{R_1/r_{be3}}{r_{e1} + r_{e2}} \quad (18)$$


- to maximise the gain of this circuit we need to make both  $R_1$  and  $r_{be3}$  as large as possible.

It is tempting to think that we might also aim to reduce the  $r_{e1} + r_{e2}$  term but remember that  $r_e = 1/g_m$  and  $g_m = eI_C/kT$ . This means that to reduce  $r_e$  one must increase  $I_C$ . Since dc conditions demand  $I_{C1}R_1 = 0.7$  V, an increase in  $I_{C1}$  would have to be accompanied by a decrease in  $R_1$  giving no net gain advantage. Input bias currents ( $I_{B1}$  and  $I_{B2}$ ) would also be adversely affected.

The input resistance of the circuit of figure 11 is given by (9) remembering that in this case  $R_E$  must be replaced by  $r_{e2}$


$$r_i = r_{be1} + (\beta_1 + 1)r_{e2} \quad (19)$$

and if  $I_{C1} \approx I_{C2}$  and  $\beta_1 \approx \beta_2$ , i.e.,  $T_1$  and  $T_2$  are balanced and identical,  $r_i \approx 2r_{be1}$ .

 

**Figure 10**

The circuit diagram of the input stage in the basic op-amp of figure 1.

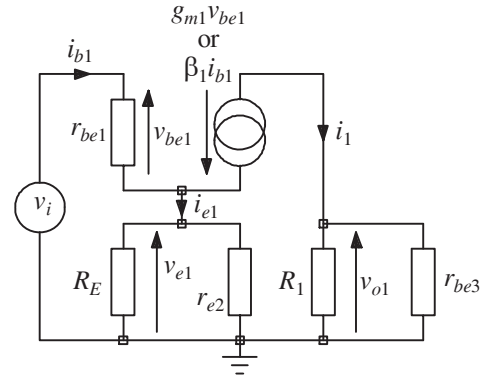

**Figure 11**

The small signal equivalent of figure 10. Note that  $T_2$  has been replaced by its common base input resistance  $r_{e2}$  and that  $r_{be3}$  is in parallel with  $R_1$ .

The remaining stages are standard circuit shapes. The  $T_3$  circuit is the standard common emitter circuit of figure 2. The base voltage is  $v_{o1}$  which was calculated (in terms of  $v_i$ ) in the input section considerations that led to (18). This means that  $R_S = 0$  (because its effects were taken into account in the calculation of  $v_{o1}$ ). The effective  $R_L$  is  $R_{VA}$  in parallel with  $r_{ce}$  of  $T_3$ ,  $r_i$  of  $T_4$  and  $r_i$  of  $T_5$ . In the circuit of figure 1,  $R_{VA}$  will be much smaller than  $r_{ce3}$ ,  $r_{i4}$  and  $r_{i5}$  so the parallel combination  $\approx R_{VA}$ . The  $T_3$  stage gain will thus be (from (3) with  $R_S = 0$ )

$$\frac{v_a}{v_{o1}} \approx -g_m R_{VA} \quad (20)$$

The output stage,  $T_4$  and  $T_5$  are emitter follower circuits connected together in what is known as a double ended or push-pull arrangement.  $T_4$  is an n-p-n transistor and is active during positive half cycles when current must flow from the positive power supply via  $T_4$  to the load.  $T_5$  is a p-n-p transistor and is active during negative half cycles when current flows from ground through the load and  $T_5$  to the negative supply. The emitter follower gain is very close to unity as shown by (12) and this leads to an overall amplifier gain

$$\frac{v_{o4}}{v_i} = \frac{v_{o4}}{v_a} \times \frac{v_a}{v_{o1}} \times \frac{v_{o1}}{v_i} = \frac{R_1 // r_{be3}}{r_{e1} + r_{e2}} g_m R_{VA} \quad (21)$$

and for an amplifier circuit such as figure 1 this gain will be in the low thousands. A general purpose commercial op-amp will have a gain larger than this figure by a factor of two to three orders of magnitude. The next section looks at how the basic circuit of figure 1 can be refined to improve the gain and other parameters.

## Refinements to the basic op-amp circuit of figure 1

### Problems with the circuit of figure 1

#### Input stage

- 1 In the input stage, half the signal is wasted because the collector of  $T_2$  is connected directly to the negative supply rail.
- 2 There is also a potential problem with collector current imbalance between  $T_1$  and  $T_2$  which will give rise to offset errors.
- 3 The input bias current is high and the input resistance is low in comparison with commercial general purpose op-amps.
- 4 The effective  $R_L$  of the first stage is relatively low leading to a very low gain.

#### $T_3$ stage

- 5  $R_{VA}$  cannot have a large value because of the constraints imposed by dc conditions but a large value is desirable to maximise signal gain.

#### Output ( $T_4$ and $T_5$ ) stage

- 6 the input resistance of  $T_4$  and  $T_5$  is dependent on the external op-amp load (effectively the  $R_E$  of the emitter follower of figure 6) and this has a direct bearing on voltage amplification stage gain.
- 7 The output resistance of the emitter follower is dependent on its source resistance.
- 8 The output transistors in figure 1 will give rise to severe crossover distortion. Crossover



distortion is distortion to the shape of the signal that occurs when conduction transfers from one output transistor to the other.

## Solutions

### Problems 1, 2, 3 and 4

Problems 1 and 2 are usually solved by introducing a circuit called a current mirror to form an active load for  $T_1$  and  $T_2$ . There is a number of different current mirror circuits that have been devised but the one shown in figure 12 is the simplest and therefore the easiest to understand. The more complicated ones were devised to correct deficiencies in the basic circuit of figure 12. We will first look at the behaviour of current mirrors before looking at the current mirror - differential pair combination.

$T_6$  and  $T_7$  are assumed to be identical. The aim of the circuit is to draw from the load circuit the same current that is being driven into  $T_7$  by the driving source. In other words, The circuit will ideally make  $I_{C6} = I_I$ . Notice that the collector and base of  $T_7$  have been connected together and that the bases of the two transistors are connected together, as are the emitters. Thus  $V_{BE}$  will be the same for each transistor.  $I_I$  will set up a  $V_{BE}$  that is sufficient to make  $T_7$  conduct a collector current  $I_{C7} = I_I - 2I_B$ .

$$I_I = I_{C7} + 2I_B = I_{C7} \left( 1 + \frac{2}{h_{FE}} \right) \text{ or } I_{C7} = I_I \frac{h_{FE}}{2 + h_{FE}} \quad (22)$$

Since  $V_{BE}$  is the same for both transistors,  $I_{C6} = I_{C7}$  so (22) describes the relationship between input and mirrored currents. Even with identical transistors the accuracy of the mirroring evidently depends upon the magnitude of  $h_{FE}$ . Note that in reality there will also be an error due to mismatch between the transistors but we will not pursue that error further here.


[The effect of finite  $h_{FE}$  can be reduced by adding a third transistor as shown in figure 13. This is sometimes called an  $h_{FE}$  helper transistor (or in some circles a  $\beta$  helper transistor). If we assume that all three transistors have the same  $h_{FE}$ ,

$$I_{BH} = \frac{2I_B}{h_{FE}} \text{ so } I_I = I_{C7} + I_{BH} = I_{C7} + \frac{2I_B}{h_{FE}} = I_{C7} \left( \frac{h_{FE}^2 + 2}{h_{FE}^2} \right), \quad (23)$$


a much smaller error than that described by (22).]

The small-signal behaviour of the circuit of figure 12 is almost the same as the dc behaviour described by (22). The differences are that for small-signal,  $h_{FE}$  is replaced by  $\beta$  and  $r_{ce}$ , the small signal resistance between collector and emitter, of  $T_7$  will conduct a very small fraction of  $i_i$ , the small-signal equivalent of  $I_I$ , to ground. We will ignore this small loss of current. As far as the load is concerned  $T_6$  looks like a current source in parallel with  $r_{ce6}$ .

Figure 14 shows the circuit diagram of the improved input stage circuit. The voltage amplification stage has been included because it has a significant effect on first stage gain. The

 

**Figure 12**  
A current mirror circuit

 

**Figure 13**  
The current mirror of figure 12 with a helper transistor

main cause of imbalance between  $I_{C1}$  and  $I_{C2}$  in figure 1 is the relatively high value of  $I_{B3}$ . In figure 14  $T_8$  is added to reduce this current which becomes  $I_{B8}$ . The combination of  $T_8$  and  $T_3$  is called a "Darlington pair". Most of  $I_3$  flows through  $T_3$  so  $I_{B3} = I_3/h_{FE3}$  as before.  $I_{B3}$  forms the emitter current of  $T_8$  so  $I_{B8} \approx I_{B3}/h_{FE8}$ . If the  $h_{FE}$ s of  $T_3$  and  $T_8$  are of the order of hundreds, the addition of  $T_8$  reduces the bias current requirement of the voltage amplification stage by at least two orders of magnitude and  $I_{C1}$  is much closer to  $I_{C2}$  as a result.

The Darlington pair of  $T_8$  and  $T_3$  also increases the input resistance of the voltage amplification stage.  $T_8$  is an emitter follower connection with an effective  $R_E$  equal to the input resistance of  $T_3$ ,  $r_{be3}$ . (13) gives the input resistance of an emitter follower and if the terms are modified for the circuit of figure 14, the input resistance looking into the base of  $T_8$  is

$$r_{i8} = r_{be8} + (\beta_8 + 1)r_{be3} \quad (24)$$

If the small-signal current gain of  $T_8$  is in the hundreds,  $r_{i8}$  will be at least two orders of magnitude bigger than  $r_{be3}$ .

The addition of  $T_8$  therefore helps to alleviate problems 2 and 3 and contributes to alleviating problem 4.

The current mirror also plays an important role in the input stage bias current balance and is also important from a signal point of view because the mirroring action works on ss changes as well as the static dc conditions. Consider the behaviour of the circuit of figure 14 when the voltage between the bases of  $T_1$  and  $T_2$  is zero.  $I_E$  splits between  $T_1$  and  $T_2$  to give collector currents of  $I_{C1}$  and  $I_{C2}$  respectively. The current  $I_{C2}$  instead of being returned directly to the negative supply as it is in figure 10 is now mirrored such that  $I_{C6} \approx I_{C2}$ . Assuming that the mirror is perfect, i.e., that  $I_{C2} = I_{C6}$ , a current sum at the collector node of  $T_1$  gives

$$I_{C1} - I_{C6} = I_{C1} - I_{C2} = I_{B8} \quad (25)$$

and assuming negligible base currents in  $T_1$  and  $T_2$

$$I_{C1} + I_{C2} = I_E \quad (26)$$


Adding (25) and (26) gives

$$I_{C1} = \frac{I_E}{2} + \frac{I_{B8}}{2} \quad (27)$$

and subtracting (26) from (25) gives

$$I_{C2} = \frac{I_E}{2} - \frac{I_{B8}}{2} \quad (28)$$

Thus the collector currents of  $T_1$  and  $T_2$  are as balanced as they can be and if  $I_{B8}$  is small compared to  $I_{C1}$  and  $I_{C2}$  the mirror maintains an excellent balance.

 

**Figure 14**

*An improved input stage incorporating a current mirror and a Darlington pair*

When a signal is present at the input the split of  $I_E$  between  $T_1$  and  $T_2$  is modulated by the signal. Consider an instant when  $V_{BT1} > V_{BT2}$ . This will set up the conditions such that  $\Delta I$  is taken from  $I_{C1}$  and added to  $I_{C2}$  to give

$$I_{C1} \rightarrow I_{C1} - \Delta I \quad (29)$$

$$I_{C2} \rightarrow I_{C2} + \Delta I \quad (30)$$

Using the  $I_{C1}$  and  $I_{C2}$  in (27) and (28) with the added current modulation of (29) and (30), the modulated  $I_{B8}$  can be found by subtracting  $I_{C6}$  ( $= I_{C2}$ ) from  $I_{C1}$

$$I_{C1} - I_{C6} = \frac{I_E}{2} + \frac{I_{B8}}{2} - \Delta I - \frac{I_E}{2} + \frac{I_{B8}}{2} - \Delta I = I_{B8} - 2\Delta I \quad (31)$$

The mirror circuit has transferred all the collector current modulation in the differential input pair into a modulated  $I_{B8}$ . In addition, the effective load resistance seen by this node is a parallel combination of  $r_{i8}$ ,  $r_{ce1}$  and  $r_{ce6}$ .  $r_{i8}$  has been shown to be large in (24) and  $r_{ce1}$  and  $r_{ce6}$  are intrinsically large. Together, the improvements offered by  $T_8$  and the mirror improve the gain of the input stage by a factor of between 20 and 50 when compared with the circuit of figure 1. The inclusion of the mirror has contributed to problems 1, 2 and 4.

## Problems 5 and 6

Problems 5 and 6 are related in the effect they have on the voltage amplification stage. The common emitter transistor,  $T_3$ , has a gain that is directly proportional both to its transconductance and to the load resistance seen between the collector node of  $T_3$  and ground. In figure 1 this resistance consists of three main components:

- the collector emitter resistance of  $T_3$ ,  $r_{ce3}$ ,
- the resistor  $R_{VA}$  and
- the input resistance of  $T_4$  and  $T_5$

The first of these is large and is difficult (though not impossible) to make larger. The second,  $R_{VA}$  is the most serious problem. The value of  $R_{VA}$  is determined by the dc condition requirements of the voltage amplification stage and this limits its value to a few 10s of  $k\Omega$ . The difficulty is usually overcome by replacing  $R_{VA}$  by a current source, a strategy that raises the effective value of  $R_{VA}$  to the output resistance of the current source which usually approximates to the  $r_{ce}$  of the current source transistor. (The tail resistor,  $R_E$ , of the differential pair is also usually replaced by a current source so that  $I_E$  is largely independent of common mode input voltage.) The input resistance of  $T_4$  and  $T_5$  is affected by the external load connected to the op-amp and this tends to make overall gain a function of external load. This effect can be significantly reduced by the inclusion of an extra transistor,  $T_9$ , which is an emitter follower forming a Darlington connected pair with whichever of  $T_4$  or  $T_5$  is conducting. These modifications can be seen in figure 15. The input resistance of  $T_9$  can be estimated by repeated use of (13) so assuming that  $T_4$  is conducting its input resistance will be

$$r_{i4} = r_{be4} + (\beta_4 + 1)R_{L\ EXT} \quad (32)$$

where  $R_{L\ EXT}$  is the op-amp's external load resistance. The input resistance of  $T_9$  is then

$$r_{i9} = r_{be9} + (\beta_9 + 1)r_{i4} \quad (33)$$

The inclusion of the current source load and  $T_9$  will increase the voltage stage gain by at least an order of magnitude.

