

# EEE225: Analogue and Digital Electronics

## Lecture II

James E. Green


Department of Electronic Engineering  
University of Sheffield  
`j.e.green@sheffield.ac.uk`

## This Lecture


- 1 One Transistor Circuits Continued...
  - Emitter Follower or Common Collector
  - Emitter Follower Voltage Gain
  - Emitter Follower Input Resistance
  - Emitter Follower Output Resistance
  - Common Base
  - Common Base Voltage Gain
  - Common Base Input Resistance
- 2 Inside the Opamp
  - Feedback System
  - Simplified Schematic of an Opamp
  - Opamp Circuit DC Conditions
  - Differential Amplifier
- 3 Review
- 4 Bear
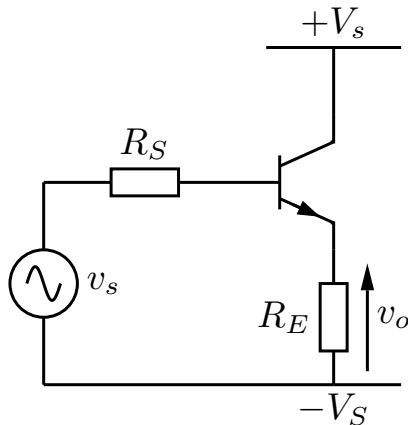
## Emitter Follower / Common Collector

- A kind of “voltage follower” or “buffer”
- Approximately unity voltage gain
- pnp or npn versions possible
- High current gain
- May be thought of as impedance transformer (so can all transistor circuits...)



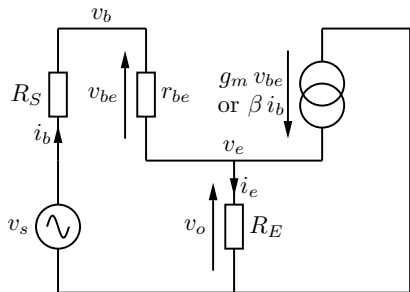In this figure the biasing circuitry is contained as an effective resistance within  $R_S$



$$v_o = v_{be} R_E \left( \frac{1}{r_{be}} + g_m \right) \quad (1)$$

$$\approx v_{be} R_E g_m \quad (2)$$

and a relation between  $v_{be}$ ,  $v_s$  and  $v_o$  is given by summing voltages around the input loop.

$$v_s = i_b R_S + v_{be} + v_o \quad (3)$$

$$= v_{be} \left( 1 + \frac{R_S}{r_{be}} \right) + v_o \quad (4)$$

using the result in (2) to eliminate  $v_{be}$ ,

$$\frac{v_o}{v_s} = \frac{r_{be} g_m R_E}{r_{be} g_m R_E + R_S + r_{be}} \quad (5)$$

$$= \frac{R_E}{\frac{1}{g_m} + \frac{R_S}{\beta} + R_E} \quad (6)$$

**1** The gain is non-inverting

**2** Gain  $\approx 1$  if  $R_E \gg R_S/\beta$  and  $R_E \gg 1/g_m$

The input resistance is given by considering  $v_b/i_b$ , recall (1)

$$v_e = v_{be} R_E \left( \frac{1}{r_{be}} + g_m \right) \quad (7)$$

and summing up the voltages...

$$v_b = v_{be} + v_e \quad (8)$$

$$= v_{be} + v_{be} R_E \left( \frac{1}{r_{be}} + g_m \right) \quad (9)$$

$$= v_{be} \left( 1 + R_E \left( \frac{1}{r_{be}} + g_m \right) \right) \quad (10)$$

since  $v_{be} = i_b r_{be}$  and  $g_m r_{be} = \beta$  we can write,

$$r_i = \frac{v_b}{i_b} = r_{be} + (\beta + 1) R_E \quad (11)$$

Generally  $(\beta + 1) R_E \gg r_{be}$  so the input resistance is dominated by the  $(\beta + 1) R_E$  term. By comparing this result with the input resistance of the non-degenerated common emitter amplifier we could show negative feedback can be used to increase the input resistance of a transistor stage.

To obtain the output resistance inject a test current  $i_t$  with the input grounded and find  $v_o/i_t$ .

Summing currents at  $v_e$


$$(1 + \beta) i_b + i_t = \frac{v_e}{R_E} \quad (12)$$

and summing up the voltages in the base loop

$$v_e = -i_b (R_S + r_{be}) \quad (13)$$

substituting (13) into (12) and solving for  $v_e/i_t$ ,
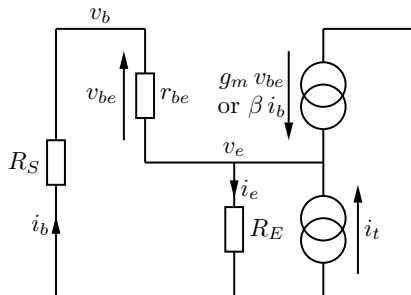
$$r_o = \frac{1}{\frac{1+\beta}{R_S+r_{be}}} + \frac{1}{R_E} \quad (14)$$





$$r_o \approx \frac{1}{g_m} + \frac{R_S}{\beta} \quad (15)$$

If  $\beta \gg 1$ , the first term becomes  $\frac{R_S+r_{be}}{\beta}$  and if  $R_E$  is large, we can ignore the  $\frac{1}{R_E}$  term.
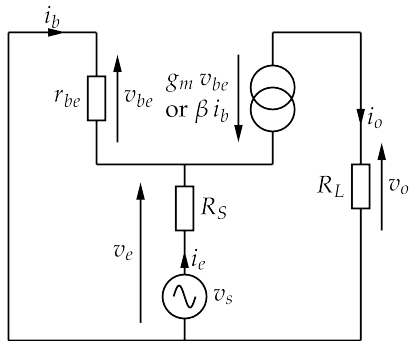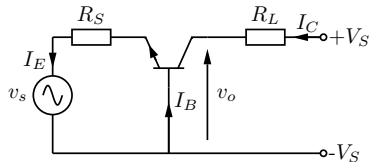
## Common Base Connection

Generally used in conjunction with other transistors in “circuit blocks”, but sometimes alone<sup>1</sup>.  $i_e$  is the input current (flowing from  $v_s$ ), since  $i_e = i_o + i_b$  the current gain ( $i_o/i_e$ ) is slightly less than 1 (actually it's  $= \alpha$ ).



summing currents,

$$i_e + i_b + g_m v_{be} = 0 \quad (16)$$

<sup>1</sup><http://dx.doi.org/10.1088/0957-0233/23/12/125901>

$$\frac{v_s - v_e}{R_S} + \frac{v_{be}}{r_{be}} + g_m v_{be} = 0 \quad (17)$$

$v_e + v_{be} = 0$  so  $v_e = -v_{be}$   
therefore (17) can be solved for  
 $v_{be}$

$$v_{be} = -\frac{v_s}{R_S \left( \frac{1}{R_S} + \frac{1}{r_{be}} + g_m \right)} \quad (18)$$

$$\approx -\frac{v_s}{1 + g_m R_S} \quad (19)$$

approximation is because  
 $1/r_{be} = g_m/\beta$  and  $\beta \gg 1$

At the output,

$$v_o = i_o R_L = -g_m v_{be} R_L \quad (20)$$

combining this with (19) to  
eliminate  $v_{be}$


$$\frac{v_o}{v_s} = \frac{g_m R_L}{1 + g_m R_S} = \frac{R_L}{r_e + R_S} \quad (21)$$

where  $r_e = 1/g_m$ .

- The gain is non-inverting
- Gain  $\propto R_L$
- If  $R_S \gg r_e$  gain controlled by ratio  $R_L/R_S$



## Common Base Input Resistance

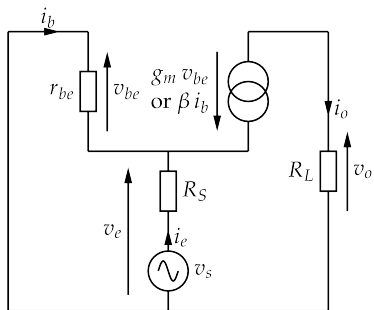

The resistance looking into the emitter,

$$r_i = \frac{v_e}{i_e} = \frac{v_e}{\frac{-v_{be}}{r_{be}} - g_m v_{be}} \quad (22)$$


Since  $v_e = -v_{be}$  and  $g_m \gg 1/r_{be}$  this reduces to  $r_i \approx \frac{1}{g_m} = r_e$ . The value is small 10s - 100s  $\Omega$

There is another model of the transistor called "T Model" in which  $r_e$  plays a much bigger role. However hybrid- $\pi$  is the only model we will use. The original  $\pi$  paper is by Giacolletto<sup>2</sup>.

<sup>2</sup><http://dx.doi.org/10.1109/JSSC.1969.1049963>
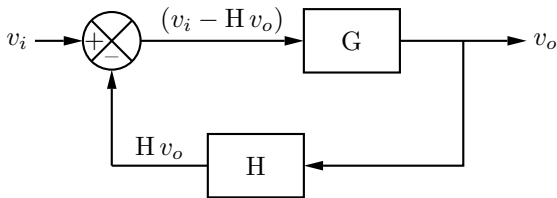
## Feedback Systems (Quick reminder)

In EEE118 we discussed the opamp in terms of a general feedback system.




$$\text{So } v_o = G (v_i - H v_o) \quad (23) \quad \text{If } |G H| \gg 1,$$

$$\text{or } v_o (1 + G H) = G v_i \quad (24)$$


$$\frac{v_o}{v_i} = \frac{G}{1 + G H} \quad (25)$$

$$\frac{v_o}{v_i} = \frac{G}{G H} = \frac{1}{H} \quad (26)$$

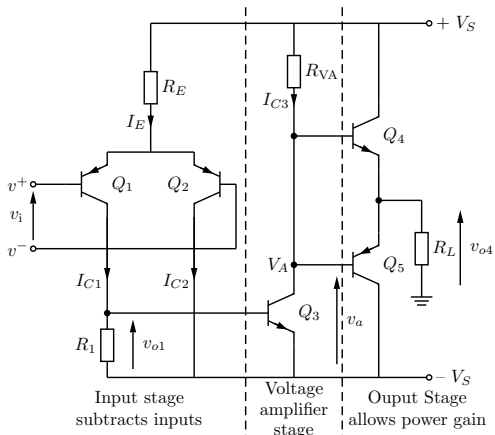
System dependent on H, designer controls  $H$  with ratio of resistors.



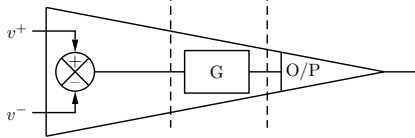
- Input stage: differential amplifier or “long tailed pair”. Subtracts the inputs.
- Voltage amplifier stage (VAS): common emitter amplifier. Provides majority of voltage gain.
- Output stage: emitter follower. Increases current capability of VAS (voltage  $\times$  current = power... hence “power gain”).



- Opamp will not work properly without feedback. Feedback controls the gain of the circuit but also helps define the DC conditions. Feedback adjusts  $v_i$  in order to achieve the internal voltage drops required for proper operation. If  $v_o = 0$ ,  $v_i$  will be at the value it needs to be in order to make  $v_o = 0$ . Feedback is *not* shown on prior slide.
- If  $v^+ \approx v^- \approx 0$ ,  $V_{E1}$  and  $V_{E2} \approx 0.7$  so  $I_E \approx (+V_S - 0.7)/R_E$ .
- $I_E$  splits between  $Q_1$  and  $Q_2$  to form  $I_{C1}$  and  $I_{C2}$ .
- $I_{C1}$  has two functions 1) create a voltage drop of 0.7 V across  $R_1$  in order to bias  $Q_3$  into conduction. 2) Provide the base current for  $Q_3$ .  $I_{C1}$  will be  $0.7/R_1 + I_{C3}/h_{FE3}$ .
- The value of  $I_{C3}$  varies with  $V_A$  and hence with  $V_{o4}$  but assuming  $V_A = 0$ ,  $I_{C3} = +V_S/R_{VA}$ .
- $I_{C2}$  is returned directly to the negative supply.
- In the case where  $v^+ \approx v^- \neq 0$ , there is a common mode input voltage,  $v_{cm}$ , and  $I_E \approx (+V_S - v_{cm})/R_E$ .

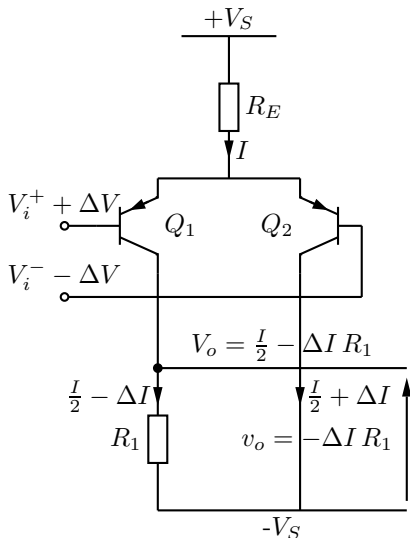


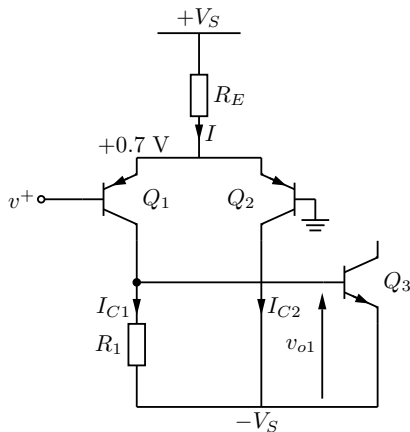- If  $v^+$  increases by  $\Delta v_i$  and  $v^-$  decreases by  $\Delta v_i$ , the average of  $v^+$  and  $v^-$  is unchanged so  $I_E$  is unchanged because  $V_{be}$  is unchanged.
- If  $v^+$  and  $v^-$  increase or decrease by  $\Delta v_i$ ,  $v_i$  is called a “common mode signal” ideally the differential amplifier will not amplify any common mode component of the input.



We must consider the effects of three transistors.  $Q_1$  and  $Q_2$  are the input differential pair.

$Q_3$  must also be considered now because its input resistance forms part of  $Q_1$ 's collector load resistance. If the input signal is regarded as  $v^+$  with respect to ground,  $Q_2$  looks like a common base connection and can be represented by its common base input resistance  $1/g_{m2}$ . The collector current of  $Q_1$  sees two resistors in parallel,  $R_1$  and the input resistance of  $Q_3$ .  $Q_3$  is a common emitter amplifier *without* degeneration. Its input resistance is  $r_{be3}$ .

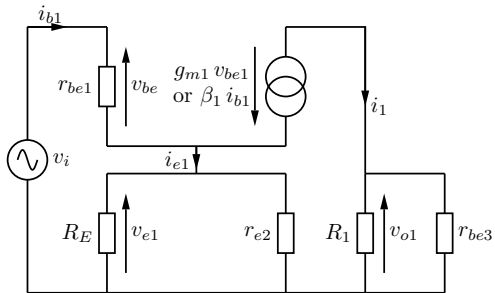

A small signal equivalent circuit describes the three transistor circuit block according to our simplifications.

This small signal model is very similar to the common emitter *with* degeneration from Lecture 1. In this case  $R_S = 0$  and  $R_E$  and  $R_L$  are parallel combinations  $R_E // r_{e2}$  and  $R_1 // r_{be3}$ . Since  $R_E \gg r_{e2}$ ,  $r_{e2}$  dominates. The gain expression for the circuit is (based on the degenerated CE analysis)

$$\frac{v_{o1}}{v_i} = -\frac{R_1 // r_{be3}}{r_{e1} + r_{e2}} \quad (27)$$

## Review

- Considered the emitter follower circuit (voltage gain, current gain, input and output resistances).
- Considered the common base circuit (voltage gain, current gain, input resistance).
- Recapped the idea of the opamp as a feedback system.
- Introduced a simplified schematic of an opamp.
- Developed some ideas around the DC conditions of the simplified opamp
- Looked at the combination of three transistors into a differential amplifier + common emitter stage and considered their combined effect.



